



CS 223 Digital Design

**Bilkent University
Fall 2023-2023**

Laboratory Assignment 3 Preliminary Report

Section 1

**Mehmet Akif Şahin
22203673**

Sun. October 15th, 2023

b) [5] Behavioral SystemVerilog module for 2-to-4 decoder and a testbench for it.

Module

```
module decoder_2to4_behav(  
    input a[1:0],  
    output y[3:0]  
);  
    assign y[0] = ~a[1] & ~a[0];  
    assign y[1] = ~a[1] & a[0];  
    assign y[2] = a[1] & ~a[0];  
    assign y[3] = a[1] & a[0];  
endmodule
```

Testbench

```
module tb_decoder_2to4(  
  
);  
    reg a[1:0];  
    wire y[3:0];  
    decoder_2to4_behav uut (a[1:0], y[3:0]);  
  
    initial begin  
        a[0] = 0;  
        a[1] = 0;  
        #10;  
        a[0] = 1;  
        a[1] = 0;  
        #10;  
        a[0] = 0;  
        a[1] = 1;  
        #10;  
        a[0] = 1;  
        a[1] = 1;  
        #10;  
    end  
endmodule
```

c) [5] Behavioral SystemVerilog module for 2-to-1 multiplexer.

Module

```
module mux_2to1_behav(  
    input a[1:0],  
    input s,  
    output y  
);  
  
    assign y = a[1] & s || a[0] && ~s;  
endmodule
```

Testbench

```
module tb_mux_2to1(  
  
    );  
    reg a[1:0], s;  
    wire y;  
  
    mux_2to1_behav uut (a[1:0], s, y);  
  
    initial begin  
        a[0] = 0;  
        a[1] = 0;  
        s = 0;  
        #10;  
        a[0] = 0;  
        a[1] = 0;  
        s = 1;  
        #10;  
        a[0] = 1;  
        a[1] = 0;  
        s = 0;  
        #10;  
        a[0] = 1;  
        a[1] = 0;  
        s = 1;  
        #10;  
        a[0] = 0;  
        a[1] = 1;  
    end
```

```
s = 0;  
#10;  
a[0] = 0;  
a[1] = 1;  
s = 1;  
#10;  
a[0] = 1;  
a[1] = 1;  
s = 0;  
#10;  
a[0] = 1;  
a[1] = 1;  
s = 1;  
#10;  
end  
endmodule
```

d) [5] Behavioral SystemVerilog module for 4-to-1 multiplexer by using three 2-to-1 multiplexer.


Module

```
module mux_4to1(  
    input a[3:0],  
    input s[1:0],  
    output y  
);  
  
    wire y_intermediate[1:0];  
  
    mux_2to1_behav mux1 (a[1:0], s[0], y_intermediate[0]);  
    mux_2to1_behav mux2 (a[3:2], s[0], y_intermediate[1]);  
  
    mux_2to1_behav mux3 (y_intermediate[1:0], s[1], y);  
  
endmodule
```

Testbench

```
module tb_mux_4to1(  
  
);  
  
    reg a[3:0], s[1:0];  
    wire y;  
  
    mux_4to1 uut (a[3:0], s[1:0], y);  
  
    initial begin  
        for (int i = 0; i < 2 ** 6; i = i + 1) begin  
            {a[3], a[2], a[1], a[0], s[1], s[0]} = i;  
            #10;  
        end  
    end  
endmodule
```

 e) [5] Schematic (block diagram) and structural System Verilog module of 8-to-1 MUX by using two 4-to-1 MUX modules, two AND gates, an INVERTER, and an OR gate. Prepare a test bench for it.



Module

```
module mux_8to1(
    input a[7:0],
    input s[2:0],
    output y
);

    reg muxouts[1:0], s2_complement, andouts[1:0];
```

```

mux_4to1 mux1 (a[3:0], s[1:0], muxouts[0]);
mux_4to1 mux2 (a[7:4], s[1:0], muxouts[1]);

not (s2_complement, s[2]);
and (andouts[0], s2_complement, muxouts[0]);
and (andouts[1], s[2], muxouts[1]);
or ( y, andouts[0], andouts[1]);
endmodule

```

Testbench

```

module tb_mux_8to1(

);


reg a[7:0], s[2:0];
wire y;

mux_8to1 uut (a[7:0], s[2:0], y);

initial begin
for (int i = 0; i < 2 ** 11; i = i + 1) begin
    {a[7], a[6], a[5], a[4], a[3], a[2], a[1], a[0], s[2], s[1], s[0]} =
i;
    #10;
end
end
endmodule

```

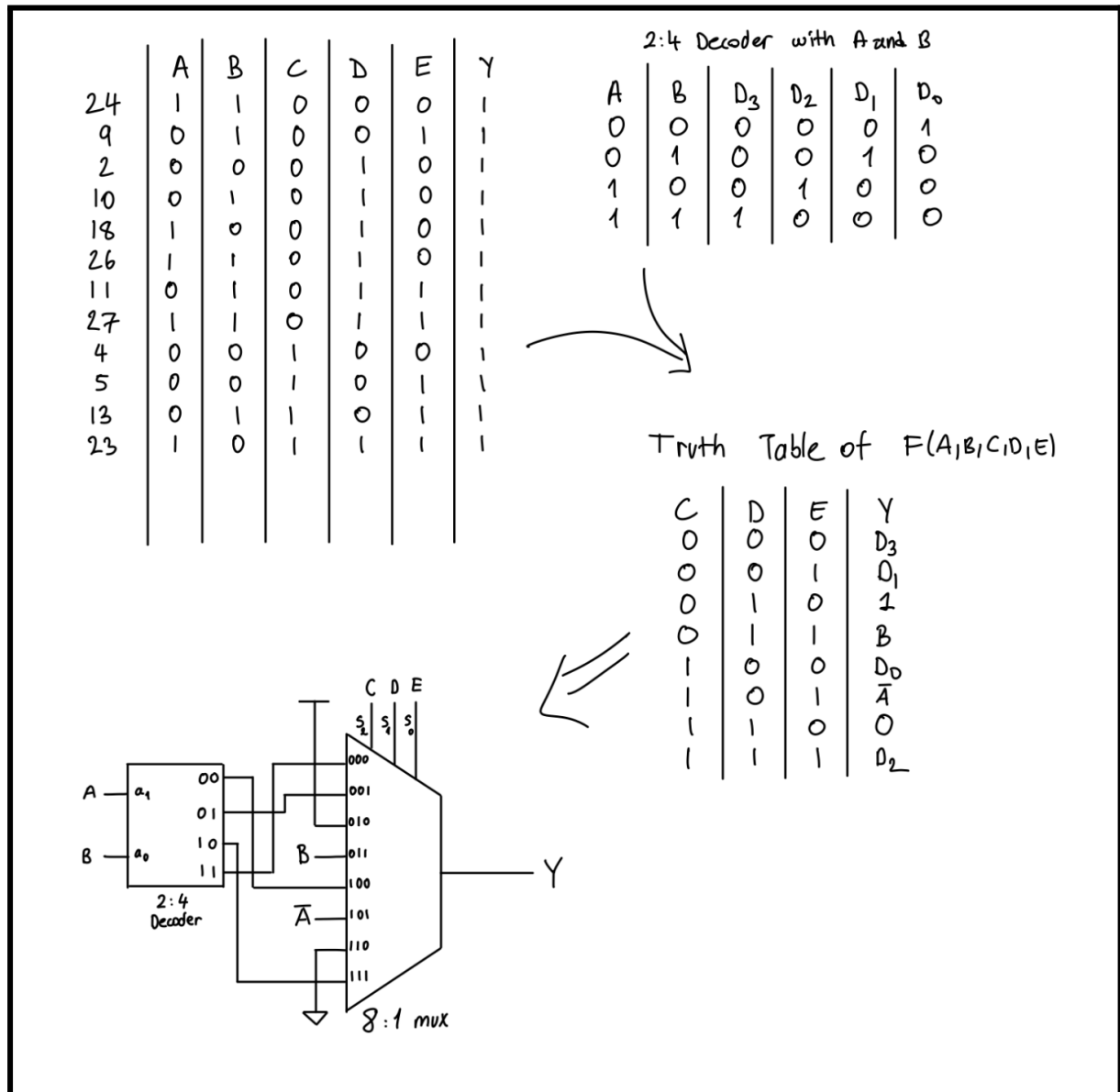f) [10] Schematic (block diagram) and SystemVerilog module for $F(A,B,C,D,E) = \sum(2,4,5,9,10,11,13,18,23,24,26,27)$ function (note that there are 12 terms), using one (not two) 8-to-1 multiplexer and a 2-to-4 decoder. Do not use any other gates (AND, OR, XOR, etc.). Your design must contain only one 8-to-1 multiplexer and one 2-to-4 decoder. Complements of signals are available.



Module

```

module my_function(
    input a, b, c, d, e,
    output y
);

```



```
    wire d_out[3:0];
    reg mux_in[7:0];

    decoder_2to4_behav decoder (.a({a, b}), .y(d_out));

    assign mux_in = {d_out[2], 1'b0, ~a, d_out[0], b, 1'b1, d_out[1],
d_out[3]};

    mux_8to1 multiplexer (.a(mux_in), .s({c, d, e}), .y(y));
endmodule
```