

CS - 223

Lab - 4 Report

Section - 1

Mehmet Akif Şahin

22203673

20.10.2023

(b) Write a SystemVerilog module for synchronously resettable D flip-flop.


```

module resettable_dflipflop
#(parameter input_width = 4)
(
    input clk,
    input [input_width-1:0] q_prime,
    input reset,
    output reg [input_width-1:0] q
);

always @ (posedge clk) begin
    if (reset) q <= 0;
    else q <= q_prime;
end
endmodule

```

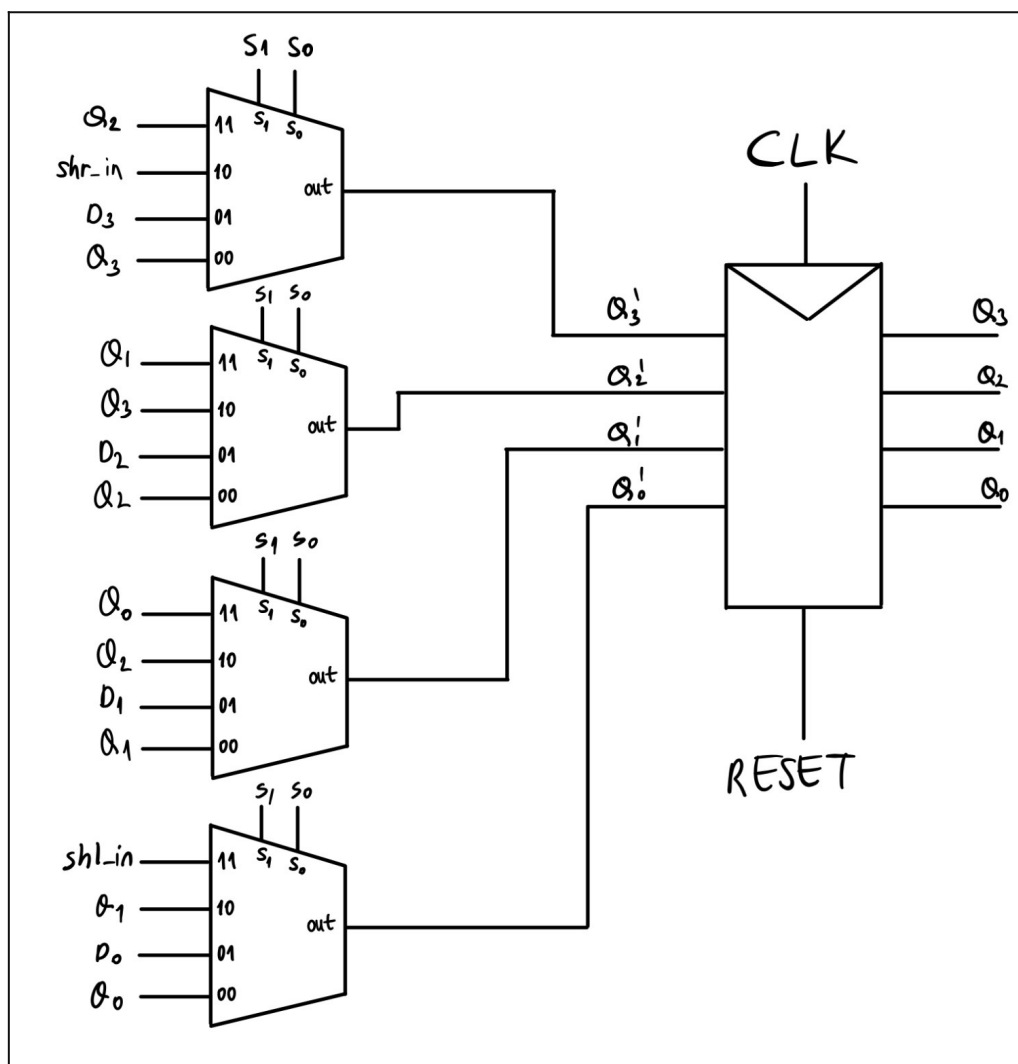(c) Draw a circuit schematic (block diagram) for the internal design of the multifunction register by using 4:1 multiplexers and synchronously resettable D flip-flops.



(d) Write a Structural SystemVerilog module for the multifunction register you designed in part (c) and a testbench for it.

Module

```
module multifunction_register(  
    input clk,  
    input [3:0] d,  
    input [1:0] s,  
    input reset,  
    input shr_in,  
    input shl_in,  
    output reg [3:0] q  
);  
  
    wire [3:0] q_prime;  
  
    mux_4to1 mux3({q[2], shr_in, d[3], q[3]}, s, q_prime[3]);  
    mux_4to1 mux2({q[1], q[3], d[2], q[2]}, s, q_prime[2]);  
    mux_4to1 mux1({q[0], q[2], d[1], q[1]}, s, q_prime[1]);  
    mux_4to1 mux0({shl_in, q[1], d[0], q[0]}, s, q_prime[0]);  
  
    resettable_dflipflop #(4) dflipflop (clk, q_prime, reset, q);  
endmodule  
  
module mux_4to1(  
    input [3:0] d,  
    input [1:0] s,  
    output y  
);  
    assign y = s[1] ? (s[0] ? d[3] : d[2]) : (s[0] ? d[1] : d[0]);  
endmodule
```

Testbench

```
module tb_mfregister(  
  
);  
  
    reg clk;  
    reg [3:0] q, d;  
    reg [1:0] s;  
    reg shr_in, shl_in;  
    reg reset;  
  
    multifunction_register uut (clk, d, s, reset, shr_in, shl_in, q);  
  
    always begin  
        clk = 1;  
        #5;  
        clk = 0;  
    end
```

```
#5;
end

initial begin
    s = 2'b01;
    d = 4'b0000;
    shr_in = 0;
    shl_in = 0;
    reset = 0;
    #30;
    s = 2'b01;
    d = 4'b0110;
    shr_in = 0;
    shl_in = 0;
    reset = 0;
    #30;
    s = 2'b10;
    d = 4'b0000;
    shr_in = 1;
    shl_in = 0;
    reset = 0;
    #30;
    s = 2'b10;
    d = 4'b0000;
    shr_in = 0;
    shl_in = 0;
    reset = 0;
    #30;
    s = 2'b11;
    d = 4'b1010;
    shr_in = 0;
    shl_in = 1;
    reset = 1;
    #30;
    s = 2'b01;
    d = 4'b0011;
    shr_in = 0;
    shl_in = 1;
    reset = 0;
    #30;
    s = 2'b11;
    d = 4'b0000;
    shr_in = 0;
    shl_in = 1;
    reset = 0;
    #30;
    s = 2'b11;
    d = 4'b0000;
    shr_in = 0;
    shl_in = 0;
    reset = 0;
    #30;
```

```
s = 2'b11;  
d = 4'b100;  
shr_in = 1;  
shl_in = 1;  
reset = 1;  
#30;  
s = 2'b01;  
d = 4'b1111;  
shr_in = 0;  
shl_in = 0;  
reset = 0;  
#30;  
end  
endmodule
```