



# **CS 223 Digital Design**

**Bilkent University  
Fall 2023-2023**


## **Laboratory Assignment 2 Preliminary Report**

### **Section 2**

**Mehmet Akif Şahin  
22203673**

**Sun. October 8th, 2023**


**b) Circuit schematic for full adder**

 

**IC List:** 1 7408 Quad-2 input AND gate, 1 7432 Quad-2 input OR gate, 1 7486 Quad-2 input XOR gate.

**Vcc and GND connections:** 7408, 7432, 7486 - 14. pin for Vcc and 7. pin for GND.

 
**c) Circuit schematic for full subtractor**



**IC List:** 1 7404 Hex-Inverting gate, 1 7408 Quad-2 input AND gate, 1 7432 Quad-2 input OR gate, 1 7486 Quad-2 input XOR gate.

**Vcc and GND connections:** 7404, 7408, 7432, 7486 - 14. pin for Vcc and 7. pin for GND.

d) Circuit schematic for 2-bit adder

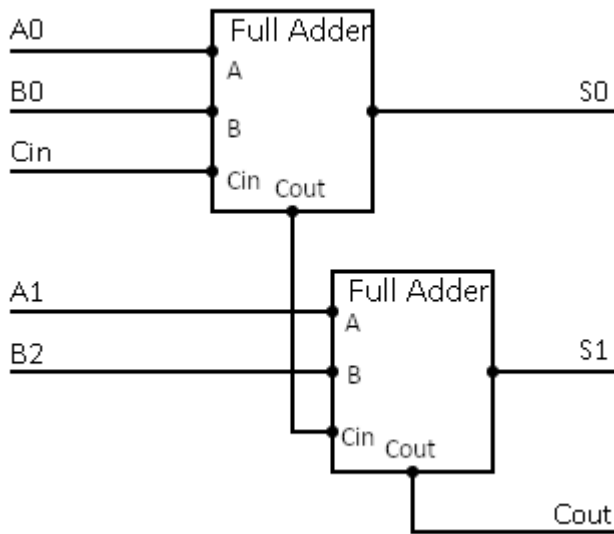

(e) Behavioral SystemVerilog module for the full adder and a testbench for it.

#### Module

```
module full_adder_behavioral(  
    input a,  
    input b,  
    input cin,  
    output sum,  
    output cout  
);  
    assign sum = a ^ b ^ cin;  
    assign cout = (a & b) | ((a ^ b) & cin);  
endmodule
```

#### Testbench

```
module tb_full_adder_behavioral();  
    logic a, b, cin, sum, cout;  
    full_adder_behavioral uut (a, b, cin, sum, cout);  
  
    initial begin  
        a=0;  
        b=0;  
        cin=0;  
        #10;  
        a=1;  
        b=0;  
        cin=0;  
        #10;  
        a=0;  
        b=1;  
    end
```

```

    cin=0;
    #10;
    a=1;
    b=1;
    cin=0;
    #10;
    a=0;
    b=0;
    cin=1;
    #10;
    a=1;
    b=0;
    cin=1;
    #10;
    a=0;
    b=1;
    cin=1;
    #10;
    a=1;
    b=1;
    cin=1;
    #10;
end
endmodule

```

**(f)** Structural SystemVerilog module for the full adder and a testbench for it.

#### **Module**

```

module full_adder_structural(
    input a,
    input b,
    input cin,
    output sum,
    output cout
);
    logic sum1, cout1, cout2;
    half_adder first_half_adder (.a(a), .b(b), .sum(sum1), .cout(cout1));
    half_adder second_half_adder (.a(cin), .b(sum1), .sum(sum), .cout(cout2));
    or (cout, cout1, cout2);
endmodule

module half_adder(
    input a,
    input b,
    output sum,
    output cout
);

```

```
xor (sum, a, b);  
and (cout, a ,b);  
endmodule
```

### Testbench

```
module tb_full_adder(  
  
);  
  logic a, b, cin, sum, cout;  
  full_adder_structural uut (a, b, cin, sum, cout);  
  
  initial begin  
    a=0;  
    b=0;  
    cin=0;  
    #10;  
    a=1;  
    b=0;  
    cin=0;  
    #10;  
    a=0;  
    b=1;  
    cin=0;  
    #10;  
    a=1;  
    b=1;  
    cin=0;  
    #10;  
    a=0;  
    b=0;  
    cin=1;  
    #10;  
    a=1;  
    b=0;  
    cin=1;  
    #10;  
    a=0;  
    b=1;  
    cin=1;  
    #10;  
    a=1;  
    b=1;  
    cin=1;  
    #10;  
  end  
endmodule
```

(g) Structural SystemVerilog module for the full subtractor and a testbench for it.

### Module

```
module full_subtractor(
    input a,
    input b,
    input bin,
    output diff,
    output bout
);
    logic diff1, bout1, bout2;
    half_subtractor first_half_subtractor (.a(a), .b(b), .diff(diff1), .bout(bout1));
    half_subtractor second_half_subtractor (.a(diff1), .b(bin), .diff(diff), .bout(bout2));
    or (bout, bout1, bout2);
endmodule

module half_subtractor(
    input a,
    input b,
    output diff,
    output bout
);
    logic a_complement;
    xor (diff, a, b);
    not (a_complement, a);
    and (bout, a_complement, b);
endmodule
```

### Testbench

```
module tb_full_subtractor(
);
    logic a, b, bin, diff, bout;
    full_subtractor uut (a, b, bin, diff, bout);

    initial begin
        a=0;
        b=0;
        bin=0;
        #10;
        a=1;
        b=0;
        bin=0;
        #10;
        a=0;
        b=1;
        bin=0;
        #10;
        a=1;
        b=1;
    end
endmodule
```

```

        bin=0;
        #10;
        a=0;
        b=0;
        bin=1;
        #10;
        a=1;
        b=0;
        bin=1;
        #10;
        a=0;
        b=1;
        bin=1;
        #10;
        a=1;
        b=1;
        bin=1;
        #10;
    end
endmodule

```

**(h)** Structural SystemVerilog module for the 2-bit adder and a testbench for it. Use the full adder module you wrote in part (f).

### Module

```

module two_bit_adder(
    input a[1:0],
    input b[1:0],
    input cin,
    output sum[1:0],
    output cout
);
    logic cout1;
    full_adder_structural first_full_adder(.a(a[0]), .b(b[0]), .cin(cin), .sum(sum[0]),
    .cout(cout1));
    full_adder_structural second_full_adder(.a(a[1]), .b(b[1]), .cin(cout1), .sum(sum[1]),
    .cout(cout));
endmodule

```

### Testbench

```

module tb_two_bit_adder(

);
    logic a[1:0], b[1:0], cin, sum[1:0], cout;
    two_bit_adder uut (.a(a[1:0]),.b(b[1:0]),.cin(cin),.sum(sum),.cout(cout));

```

```
initial begin
  for (int i = 0; i < 32; i = i + 1) begin
    {a[1], a[0], b[1], b[0], cin} = i;
  end
end
endmodule
```